

## LAB MANUAL #6

### Objectives:

- To learn and understand the working of NAND gate and NOR gate


### Introduction to NAND Gate

**74LS00 IC** contains four 2-input NAND gates. The function table and connection diagram for this IC are shown below:

#### Function Table

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

#### Connection Diagram:

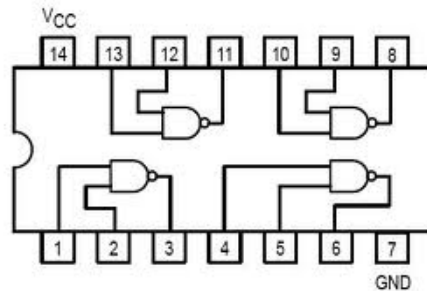

H= Logic High, L= Logic Low


### Introduction to NOR Gate

**74LS02 IC** contains four 2-input NOR gates. The function table and connection diagram for this IC are shown below:

#### Function Table:

Inputs		Output
A	B	Y
L	L	H
L	H	L
H	L	L
H	H	L

#### Connection Diagram:

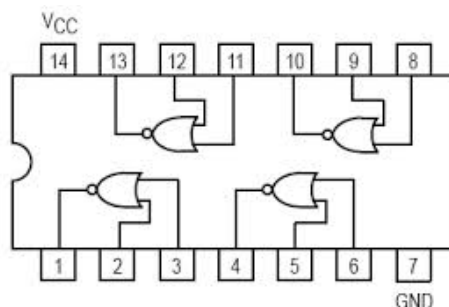

H= Logic High, L= Logic Low

### Question #1:

Simplify the Product-Of-Sums Boolean expression below.

$$\text{Out} = (A + B + C + \bar{D}) (A + B + \bar{C} + D) (A + \bar{B} + C + \bar{D}) (A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + \bar{C} + D) (\bar{A} + B + C + \bar{D}) (\bar{A} + B + \bar{C} + D)$$

### NOR and NAND Implementation on logic trainer:

#### Question#2:

Implement on **Logic Works** the following using **only** the **NAND gates**

- (a)  $Z = A.B$                       (b)  $X = A+B$                       (c) **XNOR**

#### Question#3:

Implement on **Logic Works** the following using only the **NOR gates**.

- (a)  $Z = A.B$                       (b)  $X = A+B$                       (c) **XOR**

**Question # 4:** For the Boolean function  $F1(A, B, C, D) = \sum m(2,4,12,14)$  do the following:

- a) Find truth table
- b) Find minimal SOP expression for Boolean function  $F1$  using K-map. Draw K-map.
- c) Draw the resultant expression obtained in part (b) and implement on **Logic Works** using **only NAND gates**.