

Aisha Muhammad Nawaz  
(Bscs) 202-0921 [DLD]  
Section 2E2 [LAB 8]

Question 1 Implement  $4 \times 1$  mux using one  $2 \times 4$  decoder, four ANDs and three OR gate.

$$2^n = 4 = 2^2$$

$n = 2$  (Select lines)

truth table

1  $2 \times 4$  decoder  
4 ANDs  
3 OR

Implementation  
done on  
logic works!

$S_1$	$S_0$	$F$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


## Question 2

Implement the following function using 4x1 mux.

$$F(x, y, z) = m_1 + m_2 + m_6 + m_7 \quad 2^{\textcircled{2}} = 4$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

## Diagram

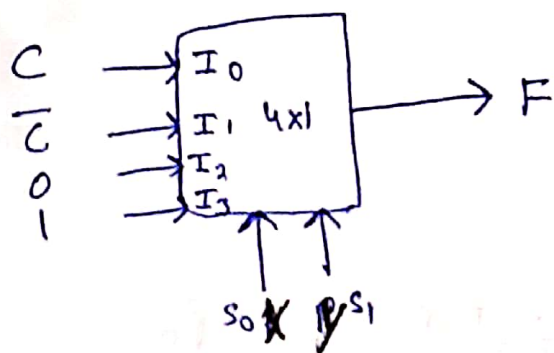

# Question 3


$A_1 A_0$  and  $B_1 B_0$   
are 2 bit numbers

$A_1 A_0 \times 2^2$

$\times B_1 B_0$

$A_1 B_0 \times 2^1 \quad A_0 B_0 \times 2^0$

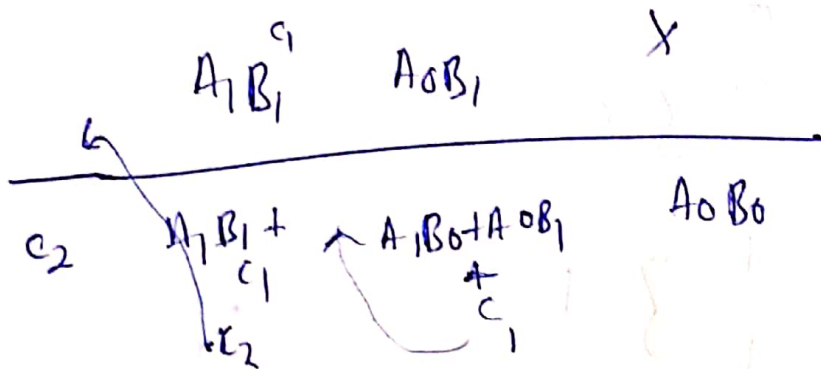\* When you multiply  
2, 2 Bit number  
max output  
is 4 Bit  
number




$$P_0 = A_0 B_0$$


$$P_1 = A_1 B_0 + A_0 B_1$$

$$P_2 = A_1 B_1 + C_1$$


$$P_3 = C_2$$

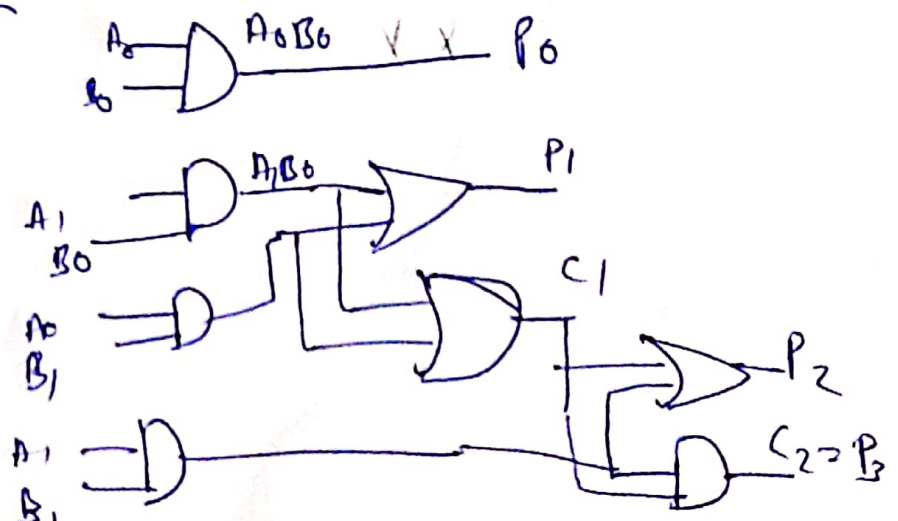


Question 1:

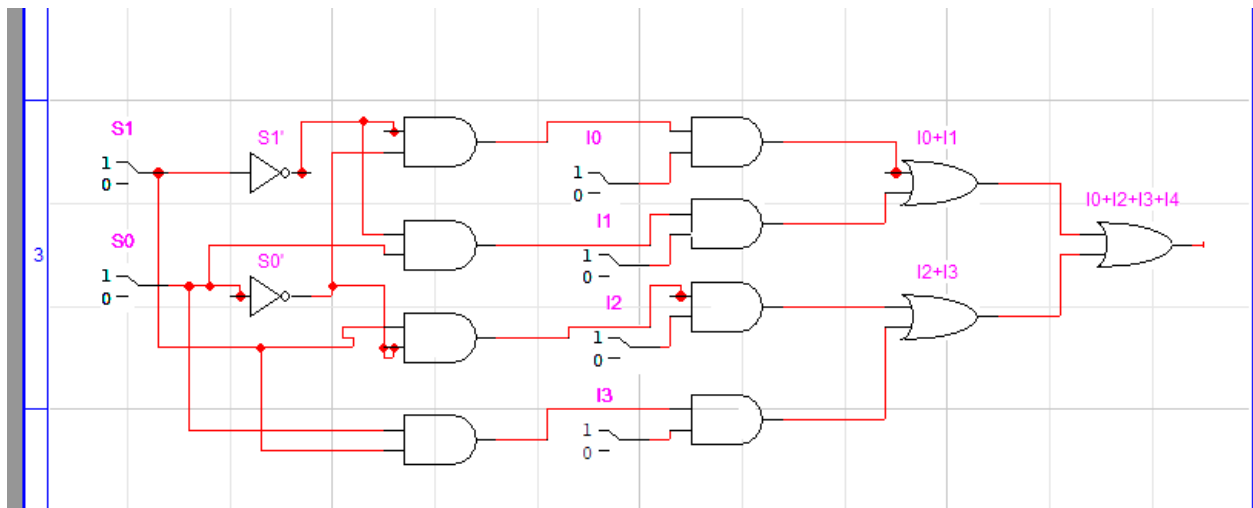

Q2:

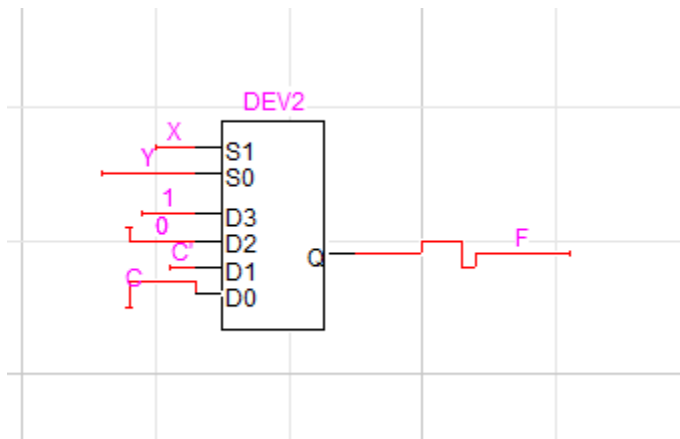

Q3:

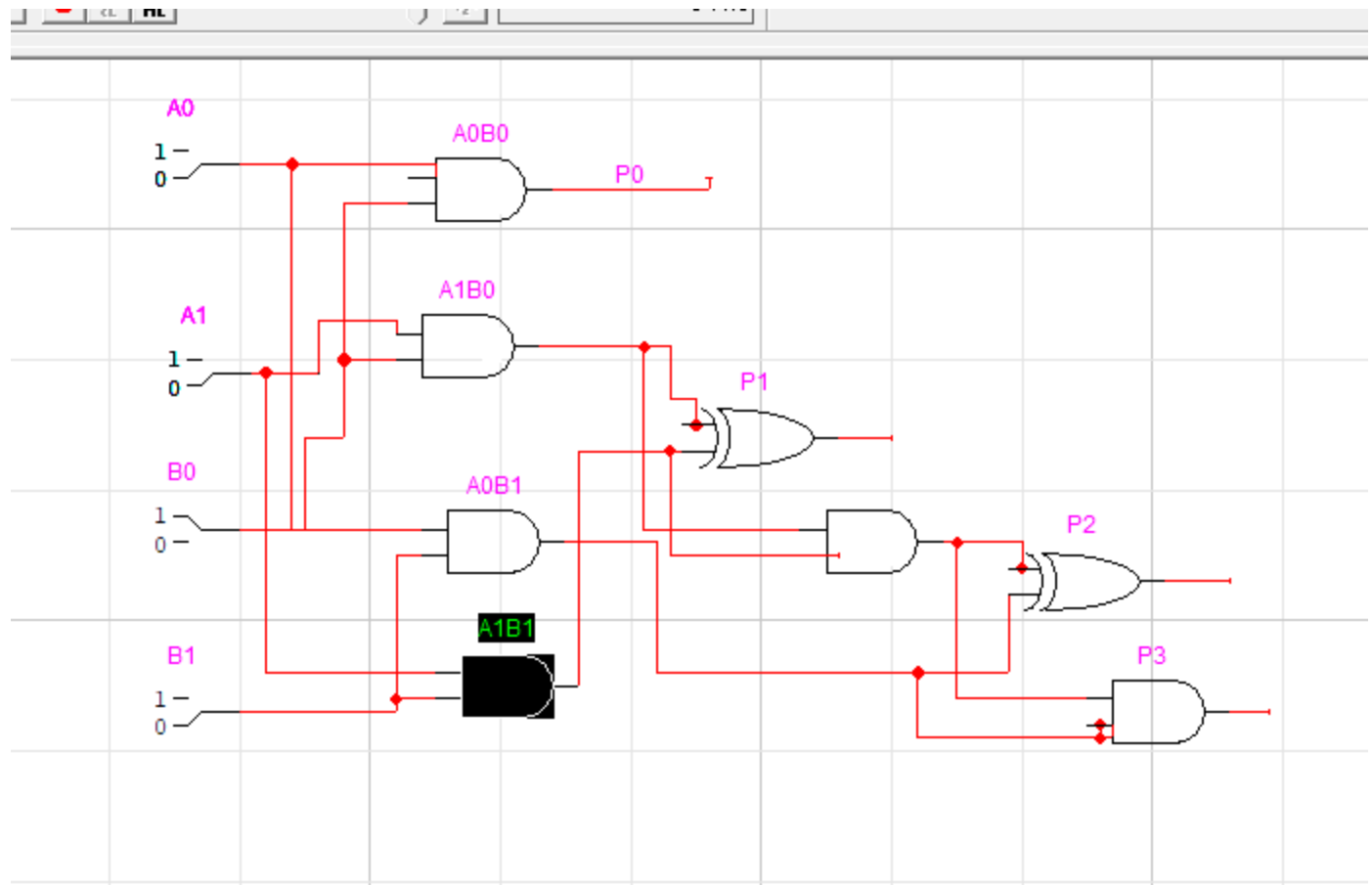

Q4:

