

# Lab Manual#12`



August 1986  
Revised March 2000

## DM74LS74A Dual Positive-Edge-Triggered D Flip-Flops with Preset, Clear and Complementary Outputs

### General Description


This device contains two independent positive-edge-triggered D flip-flops with complementary outputs. The information on the D input is accepted by the flip-flops on the positive going edge of the clock pulse. The triggering occurs at a voltage level and is not directly related to the transition time of the rising edge of the clock. The data on the D input may be changed while the clock is LOW or HIGH without affecting the outputs as long as the data setup and hold times are not violated. A low logic level on the preset or clear inputs will set or reset the outputs regardless of the logic levels of the other inputs.

### Ordering Code:

Order Number	Package Number	Package Description
DM74LS74AM	M14A	14-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-120, 0.150 Narrow
DM74LS85ASJ	M14D	14-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide
DM74LS74AN	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

### Connection Diagram

 


### Function Table


Inputs				Outputs	
PR	CLR	CLK	D	Q	$\overline{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H (Note 1)	H (Note 1)
H	H	$\uparrow$	H	H	L
H	H	$\uparrow$	L	L	H
H	H	L	X	$Q_0$	$\overline{Q}_0$

H = HIGH Logic Level  
X = Either LOW or HIGH Logic Level  
L = LOW Logic Level  
 $\uparrow$  = Positive-going Transition  
 $Q_0$  = The output logic level of Q before the indicated input conditions were established.

Note 1: This configuration is nonstable; that is, it will not persist when either the preset and/or clear inputs return to their inactive (HIGH) level.

Figure 1: D FF IC

 

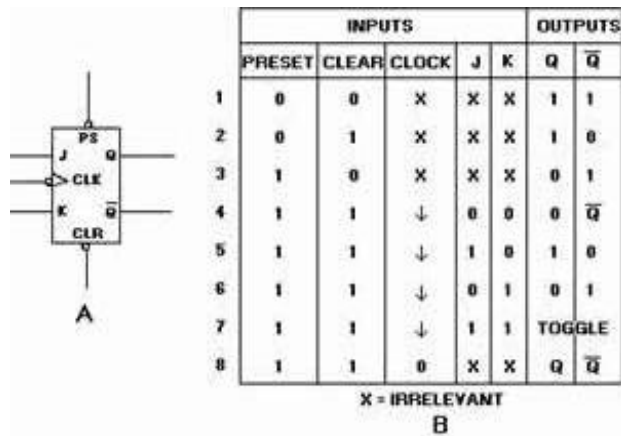

**Figure 2: JK FF IC**

**LAB Task 1:** Design and implement a master slave flip flop. Use D flip flop as master and SR as a slave in LogicWorks.

Make it operate as:

- Negative Edge Triggered
- Positive Edge Triggered

Compare and explain the timing diagram of both

**LAB Task 2:** Design and Implement a SR Master Slave Flip Flop using SR flip flops on LogicWorks with

- Negative Edge Triggered
- Positive Edge Triggered