
Lab Manual # 10

OBJECTIVE: To understand how a latch works to hold the data and set and reset states.

NOTE: Properly label the inputs and outputs in circuit diagrams & in timing diagrams

Lab Task 1:

Implement the combinational circuit of **S'R' Latch** on **logic works** using **NAND gates** and make the **truth table**.


Show the **timing diagram** also on **logic works**.

Lab Task 2:

Implement the combinational circuit of **SR Latch** on **logic works** using **NOR gates** and make the **truth table**.

Show the **timing diagram** also on **logic works**.

Timing Diagram:

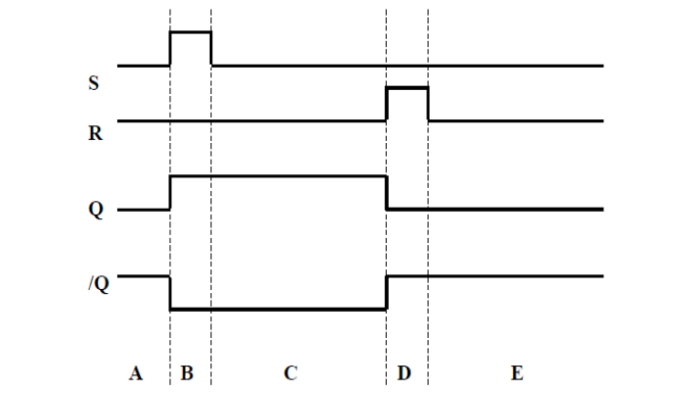

Lab Task 3:

Implement the combinational circuit of **S'R' Latch** with **Control input** on **logic works** and make the **truth table**.

Show the **timing diagram** also on **logic works**.

Timing Diagram:

