
DLD LAB MANUAL #04

Purpose of this Lab:

- Max terms and min terms
- SOP and POS
- Conversion between min terms & max-terms.


AND (74LS08)

Connection Diagram

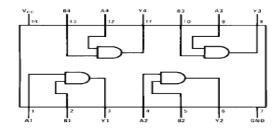


OR (74LS32)

Connection Diagram

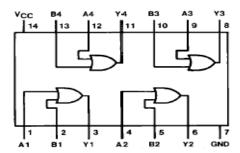

NOT (74LS04)

Connection Diagram

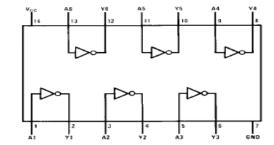

In LAB TASKS

Q1. Convert the following to **POS** form by using the **Distributive law** & implement on Logic Works.

$$xy' + yz'$$

Q2. Convert the following to POS form by using the De Morgan's laws & implement on Logic Works.

$$b'd + ac'd'$$

Q3. Write the following in **SOP** form & implement on **Logic Works**.

a.
$$(x'+y)(y'+z)$$

a.
$$(x'+y)(y'+z)$$
 b. $(x + y')(y'+z)$

Q4. For the Boolean Functions **E** and **F**:

- List min-term and max-terms of each function.
- Express E and F in sum-of-min-terms algebraic form. ii.
- iii. Implement the E function on Logic works.

X	Y	Z	E	F
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	0
1	1	1	0	1

Q5. Find Max terms from the following Min terms and write its expression. Also, implement the resultant expression on Logic Works.

$$F(X,Y,Z) = \Sigma m (1,3,6,7)$$

Q6. Find **Min terms** from the following Max terms and write its **expression**. Also, implement the resultant expression on Logic Works.

$$F(A,B,C) = \prod M(0,3,4,5,7)$$

Q7. Find Max terms from the following Min terms. Also, implement the expressions of min terms & max terms (both) on Logic Works.

$$F(X,Y,Z) = \Sigma m (0,1,2,4,6)$$

Q8. Find the output expression, truth-table. And also implement on Logic Works:

